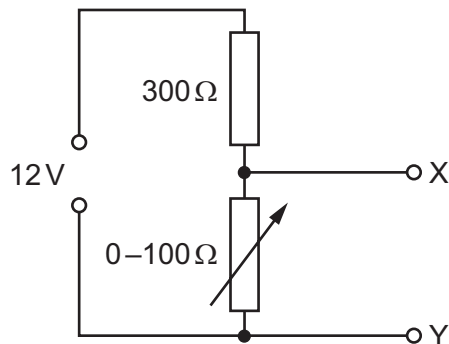


- 38** The diagram shows a potential divider connected to a 12V supply of negligible internal resistance.



Which range of voltages can be obtained between X and Y?

- A** 0 to 3V **B** 0 to 4V **C** 0 to 8V **D** 0 to 9V