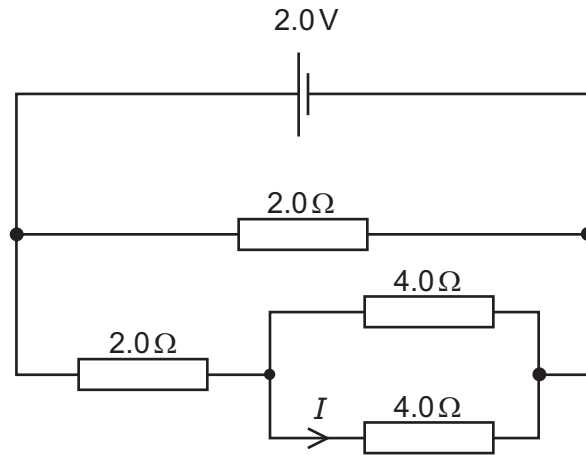


- 37** A cell of e.m.f. 2.0 V and negligible internal resistance is connected to a network of resistors as shown.



What is the current I ?

- A** 0.25 A **B** 0.33 A **C** 0.50 A **D** 1.5 A