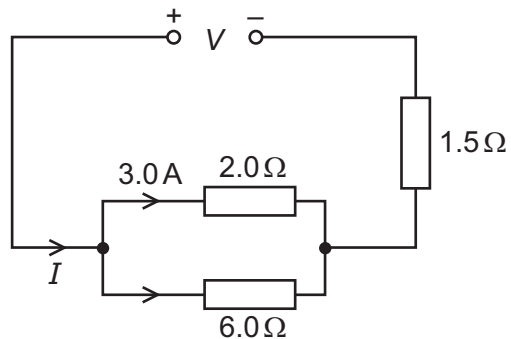


37 In the circuit shown, there is a current of 3.0 A in the 2.0Ω resistor.



What are the values of the current I delivered by the power supply and the voltage V across it?

	I/A	V/V
A	3.0	10.5
B	4.0	9.0
C	4.0	12
D	12	18