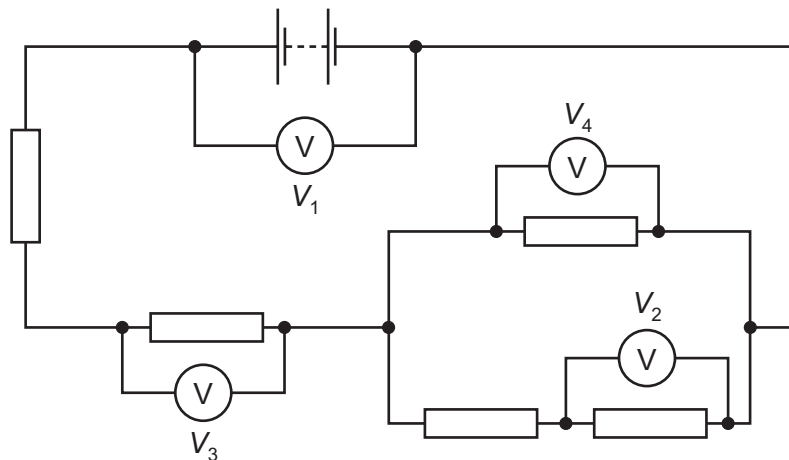


38 In the circuit shown, all the resistors are identical.



The reading V_1 is 8.0 V and the reading V_2 is 1.0 V .

What are the readings on the other voltmeters?

	V_3/V	V_4/V
A	1.5	1.0
B	3.0	2.0
C	4.5	3.0
D	6.0	4.0