

32 A charge of 8.0 C passes through a resistor of resistance $30\ \Omega$ at a constant rate in a time of 20 s .

What is the potential difference across the resistor?

A 0.40 V

B 5.3 V

C 12 V

D 75 V

Space for working