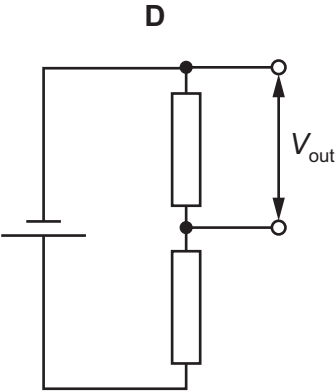
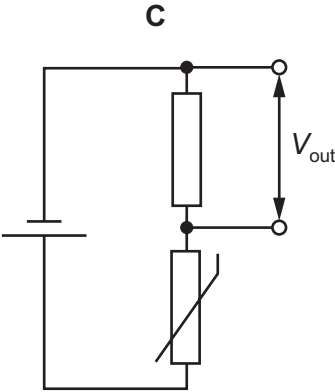
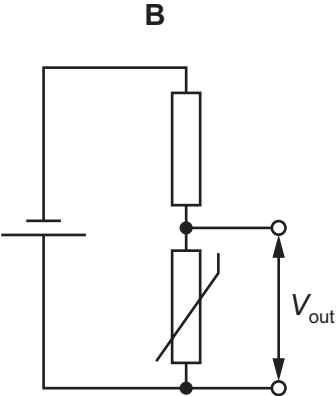
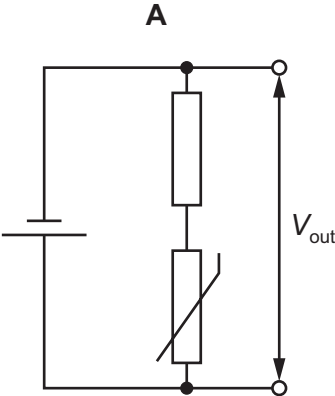


33 Which circuit results in output voltage V_{out} increasing with increasing temperature?



34 For circuit A, if resistance R is constant, then