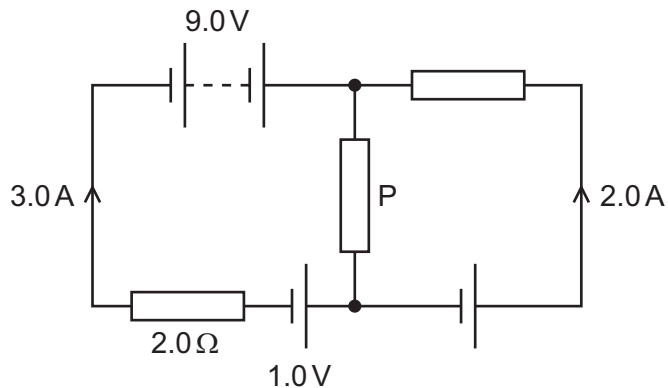


34 The diagram shows a circuit containing a battery and cells with negligible internal resistance.

Some values of current, electromotive force (e.m.f.) and resistance are shown.

One resistor is labelled P.



What is the resistance of resistor P?

- A** $0.40\ \Omega$ **B** $0.80\ \Omega$ **C** $2.0\ \Omega$ **D** $2.8\ \Omega$