

- 7 (a) Electric current is a flow of charge carriers. The charge on the carriers is quantised. Explain what is meant by *quantised*.

.....[1]

- (b) A battery of electromotive force (e.m.f.) 9.0 V and internal resistance $0.25\ \Omega$ is connected in series with two identical resistors X and a resistor Y, as shown in Fig. 7.1.

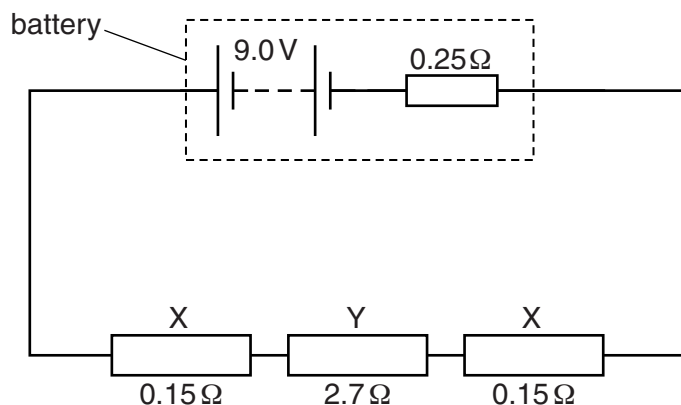


Fig. 7.1

The resistance of each resistor X is $0.15\ \Omega$ and the resistance of resistor Y is $2.7\ \Omega$.

- (i) Show that the current in the circuit is 2.8 A .

[3]

- (ii) Calculate the potential difference across the battery.

potential difference = V [2]

- (c) Each resistor X connected in the circuit in (b) is made from a wire with a cross-sectional area of 2.5 mm^2 . The number of free electrons per unit volume in the wire is $8.5 \times 10^{29} \text{ m}^{-3}$.

- (i) Calculate the average drift speed of the electrons in X.

drift speed = ms^{-1} [2]

- (ii) The two resistors X are replaced by two resistors Z made of the same material and length but with half the diameter.

Describe and explain the difference between the average drift speed in Z and that in X.

.....

[2]

[Total: 10]