

- 4 An ideal transformer has 5000 turns on its primary coil. It is to be used to convert a mains supply of 230V r.m.s. to an alternating voltage having a peak value of 9.0V.

(a) Calculate the number of turns on the secondary coil.

number = ..... [3]

- (b) The output from the transformer is to be full-wave rectified. Fig. 4.1 shows part of the rectifier circuit.

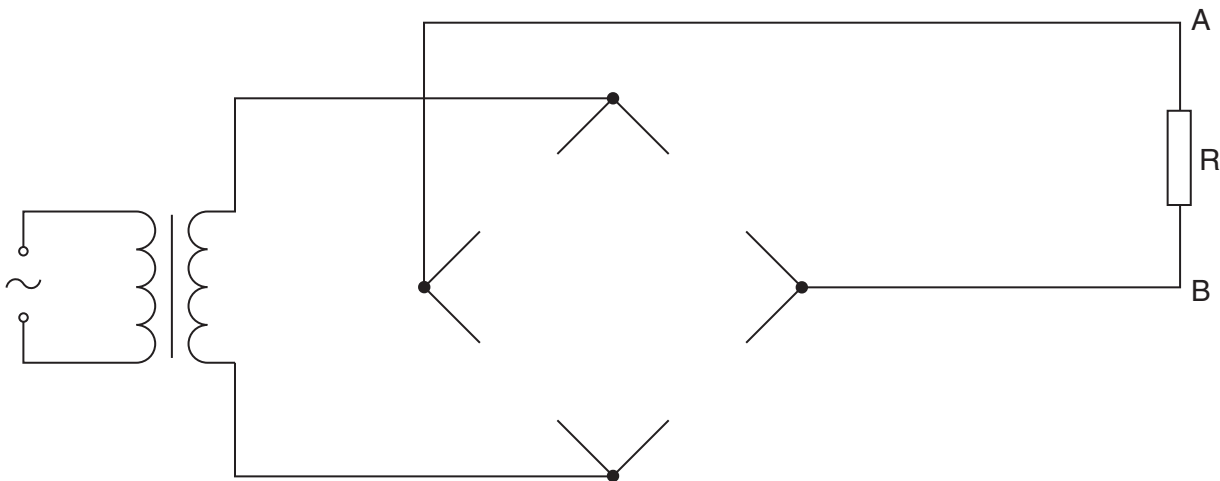


Fig. 4.1

On Fig. 4.1, draw

- (i) diode symbols to complete the diagram of the rectifier such that terminal A of the resistor R is positive with respect to terminal B, [2]
- (ii) the symbol for a capacitor connected to provide smoothing of the potential difference across the resistor R. [1]

- (c) Fig. 4.2 shows the variation with time  $t$  of the smoothed potential difference  $V$  across the resistor  $R$ .

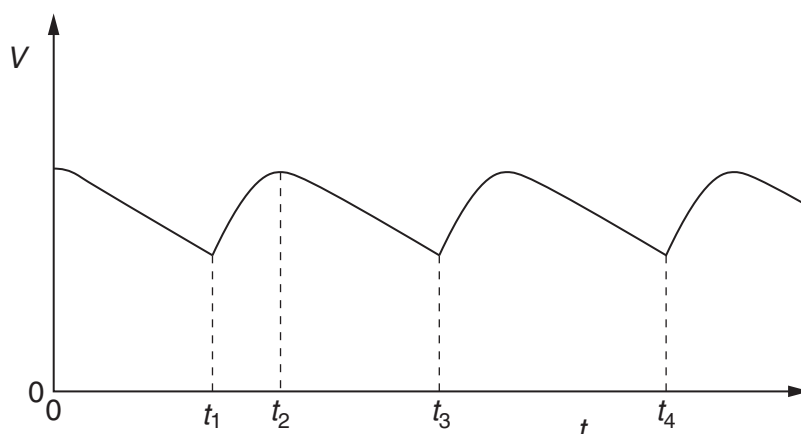


Fig. 4.2

- (i) State the interval of time during which the capacitor is being charged from the transformer.

from time ..... to time ..... [1]

- (ii) The resistance of the resistor  $R$  is doubled. On Fig. 4.2, sketch the variation with time  $t$  of the potential difference  $V$  across the resistor. [2]