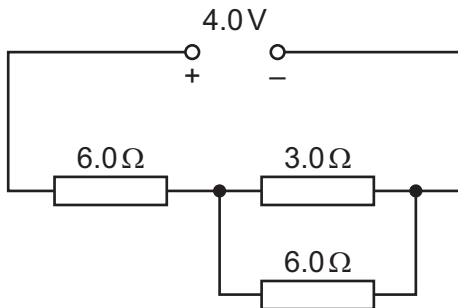


37 A network consists of a $3.0\,\Omega$ resistor and two $6.0\,\Omega$ resistors, as shown.



The potential difference (p.d.) across the network is 4.0 V.

What is the current through the $3.0\,\Omega$ resistor?

A 0.17 A

B 0.25 A

C 0.33 A

D 1.3 A