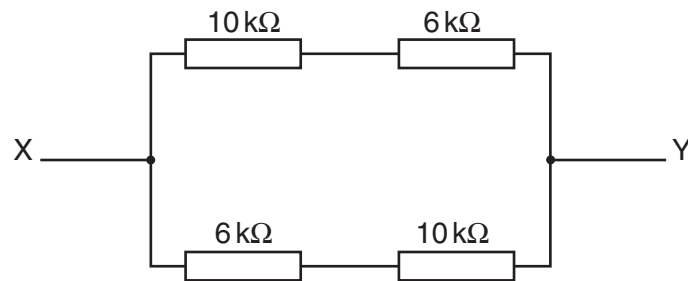


33 The diagram shows an arrangement of four resistors.



What is the resistance between X and Y?

- A** $4\text{ k}\Omega$ **B** $8\text{ k}\Omega$ **C** $16\text{ k}\Omega$ **D** $32\text{ k}\Omega$