

- 4 (a) State two functions of capacitors connected in electrical circuits.

1.

.....

2.

.....

[2]

- (b) Three capacitors are connected in parallel to a power supply as shown in Fig. 4.1.

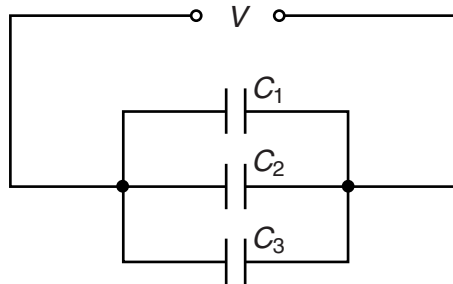


Fig. 4.1

The capacitors have capacitances C_1 , C_2 and C_3 . The power supply provides a potential difference V .

- (i) Explain why the charge on the positive plate of each capacitor is different.

.....

.....

..... [1]

- (ii) Use your answer in (i) to show that the combined capacitance C of the three capacitors is given by the expression

$$C = C_1 + C_2 + C_3.$$

[2]

- (c) A student has available three capacitors, each of capacitance $12\mu\text{F}$. Draw circuit diagrams, one in each case, to show how the student connects the three capacitors to provide a combined capacitance of

*For
Examiner's
Use*

(i) $8\mu\text{F}$,

[1]

(ii) $18\mu\text{F}$.

[1]