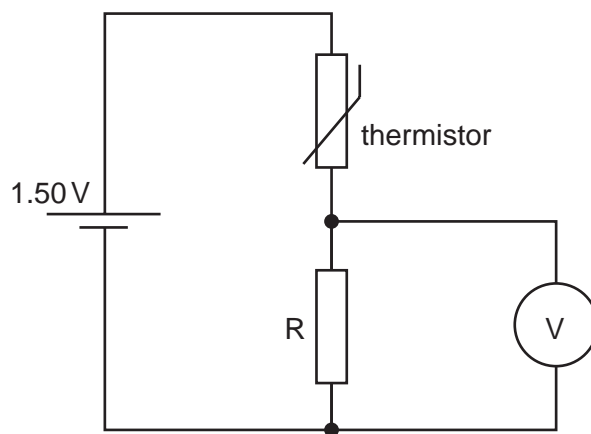


- 8** A thermistor has resistance  $3900\ \Omega$  at  $0^\circ\text{C}$  and resistance  $1250\ \Omega$  at  $30^\circ\text{C}$ . The thermistor is connected into the circuit of Fig. 8.1 in order to monitor temperature changes.



**Fig. 8.1**

The battery of e.m.f.  $1.50\ \text{V}$  has negligible internal resistance and the voltmeter has infinite resistance.

- (a)** The voltmeter is to read  $1.00\ \text{V}$  at  $0^\circ\text{C}$ . Show that the resistance of resistor  $R$  is  $7800\ \Omega$ .

[2]

- (b)** The temperature of the thermistor is increased to  $30^\circ\text{C}$ . Determine the reading on the voltmeter.

reading = ..... V [2]

- (c) The voltmeter in Fig. 8.1 is replaced with one having a resistance of  $7800\ \Omega$ . Calculate the reading on this voltmeter for the thermistor at a temperature of  $0\ ^\circ\text{C}$ .

reading = ..... V [2]





