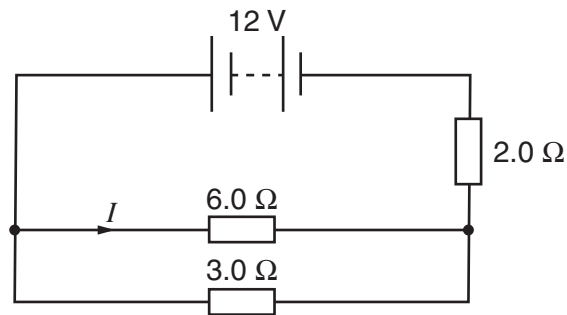


- 31 The diagram shows a circuit in which the battery has negligible internal resistance.



What is the value of the current I ?

- A** 1.0 A **B** 1.6 A **C** 2.0 A **D** 3.0 A