

34 A resistor dissipates 25 W of power when there is a potential difference (p.d.) of 4.0 V across it.

What is the resistance of the resistor?

A $0.16\ \Omega$

B $0.64\ \Omega$

C $100\ \Omega$

D $400\ \Omega$