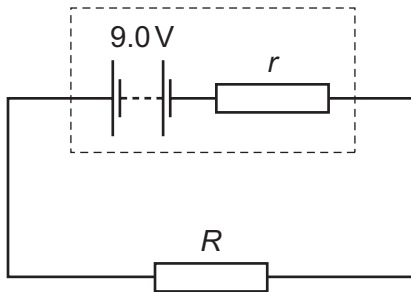


- 34** A simple circuit is formed by connecting a resistor of resistance R between the terminals of a battery of electromotive force (e.m.f.) 9.0 V and constant internal resistance r .



A charge of 6.0 C flows through the resistor in a time of 2.0 minutes causing it to dissipate 48 J of thermal energy.

What is the internal resistance r of the battery?

- A** $0.17\ \Omega$ **B** $0.33\ \Omega$ **C** $20\ \Omega$ **D** $160\ \Omega$

- 35** A source of e.m.f. 9.0 mV has an internal resistance of $6.0\ \Omega$.