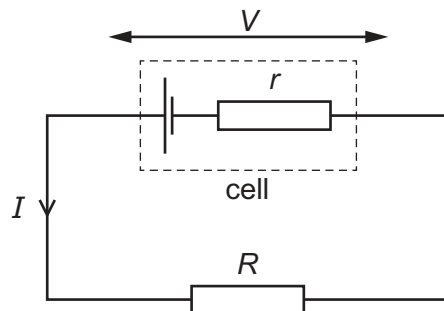


- 35** A cell of constant electromotive force drives a current I through an external resistor of resistance R . The terminal potential difference (p.d.) across the cell is V .



When the internal resistance r of the cell increases, what is the effect on V and on I ?

	V	I
A	decreases	decreases
B	decreases	increases
C	increases	decreases
D	increases	increases