

- 6 (a) State Kirchhoff's first law.

.....
 [1]

- (b) The variations with potential difference V of the current I for a resistor X and for a semiconductor diode are shown in Fig. 6.1.

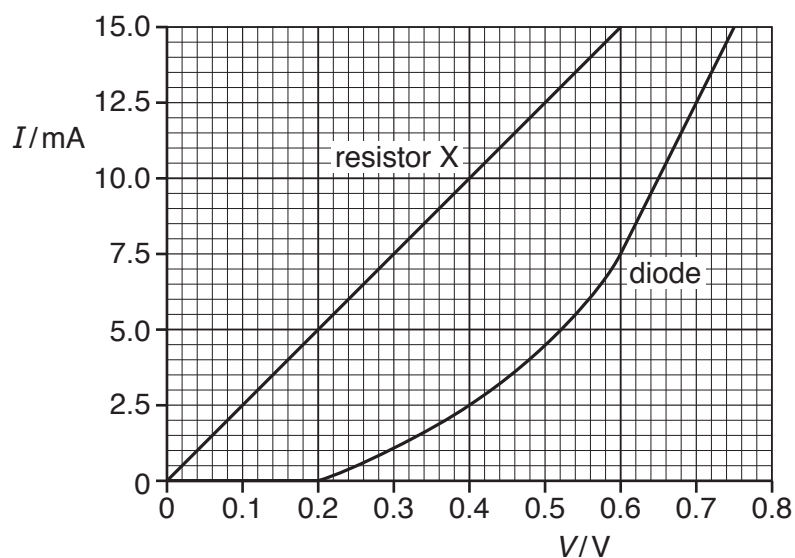


Fig. 6.1

- (i) Determine the resistance of the diode for a potential difference V of 0.60 V.

resistance = Ω [3]

- (ii) Describe, qualitatively, the variation of the resistance of the diode as V increases from 0.60 V to 0.75 V.

..... [1]

- (c) The diode and the resistor X in (b) are connected into the circuit shown in Fig. 6.2.

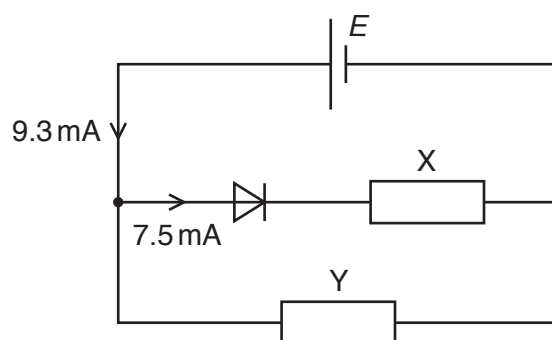


Fig. 6.2

The cell has electromotive force (e.m.f.) E and negligible internal resistance. Resistor Y is connected in parallel with resistor X and the diode. The current in the cell is 9.3 mA and the current in the diode is 7.5 mA .

- (i) Use Fig. 6.1 to determine E .

$$E = \dots\dots\dots \text{V} \quad [1]$$

- (ii) Determine the resistance of resistor Y.

$$\text{resistance} = \dots\dots\dots \Omega \quad [2]$$

- (iii) Calculate the power dissipated in the diode.

$$\text{power} = \dots\dots\dots \text{W} \quad [2]$$

- (iv) The cell is now replaced by a new cell of e.m.f. 0.50 V and negligible internal resistance. Use Fig. 6.1 to determine the new current in the diode.

$$\text{current} = \dots\dots\dots \text{mA} \quad [1]$$