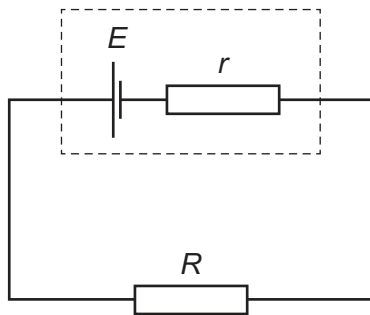


- 31** A cell of electromotive force (e.m.f.)  $E$  and internal resistance  $r$  is connected to an external resistor of resistance  $R$ , as shown.



What is the power dissipated in the external resistor?

- A**  $\frac{E^2(R+r)}{R^2}$       **B**  $\frac{E^2R}{(R+r)^2}$       **C**  $\frac{E^2(R+r)}{r^2}$       **D**  $\frac{E^2r}{(R+r)^2}$