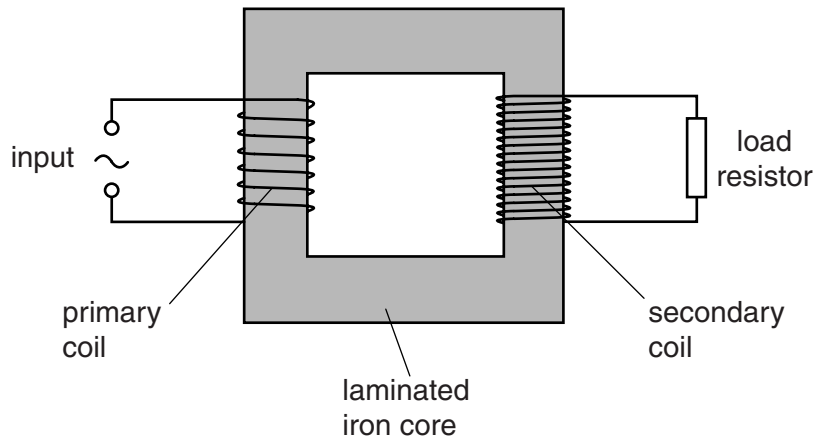


- 6 A simple transformer is illustrated in Fig. 6.1.



**Fig. 6.1**

- (a)** State

- (i)** why the iron core is laminated,

.....  
 .....  
 ..... [2]

- (ii)** what is meant by an *ideal* transformer.

.....  
 ..... [1]

- (b)** An ideal transformer has 300 turns on the primary coil and 8100 turns on the secondary coil.

The root-mean-square input voltage to the primary coil is 9.0V.

Calculate the peak voltage across the load resistor connected to the secondary coil.

peak voltage = ..... V [2]