

- 36** Four potential divider circuits each consist of a battery of electromotive force (e.m.f.) 9 V and negligible internal resistance connected to a combination of resistors. Each of the resistors in the circuits has a resistance of X or $2X$.

Which circuit has the largest output voltage V ?

