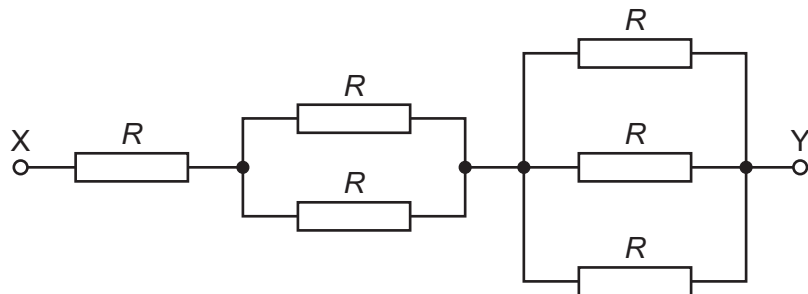


- 36** The diagram shows a network of resistors. Each resistor has resistance R .



What is the total resistance of the network between points X and Y?

A $\frac{R}{6}$

B $\frac{6R}{11}$

C $\frac{11R}{6}$

D $6R$