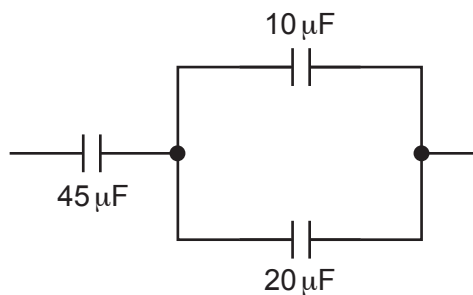


- 4 (a) Three capacitors are connected as shown in Fig. 4.1.



**Fig. 4.1**

Determine the total capacitance, in  $\mu\text{F}$ , of the network of three capacitors.


capacitance = .....  $\mu\text{F}$  [2]

- (b) A capacitor of capacitance  $45\ \mu\text{F}$  is connected to a variable power supply initially set at  $8.0\ \text{V}$ . The output of the power supply increases so that the potential difference (p.d.) across the capacitor increases to  $9.6\ \text{V}$ .

Calculate the increase in energy  $\Delta E$  stored in the capacitor.

$\Delta E = \dots\dots\dots\ \text{J}$  [2]


- (c) A sinusoidal a.c. power supply is connected to the input of a bridge rectifier. The output of the rectifier is connected to a load resistor.
- (i) Complete the circuit in Fig. 4.2 by adding a capacitor to smooth the p.d. across the load resistor.

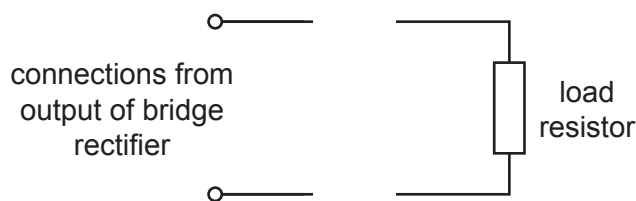

**Fig. 4.2**

[1]

(ii) The variation with time  $t$  of the p.d.  $V$  of the smoothed output is shown in Fig. 4.3.

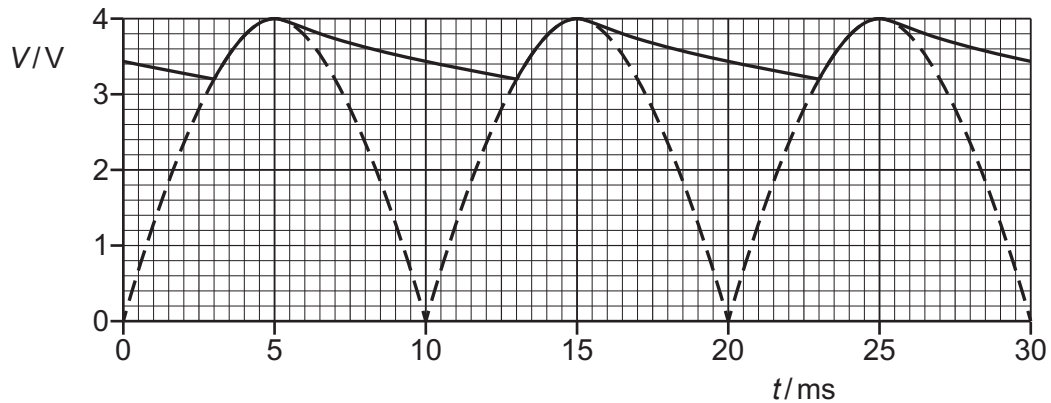

**Fig. 4.3**

Determine the time constant, in ms, of the smoothing circuit.

time constant = ..... ms [3]

(d) A sinusoidal a.c. power supply has a maximum power of 16 W.

State the value of the mean power when the output of the power supply is:

(i) full-wave rectified

mean power = ..... W [1]

(ii) half-wave rectified.

mean power = ..... W [1]