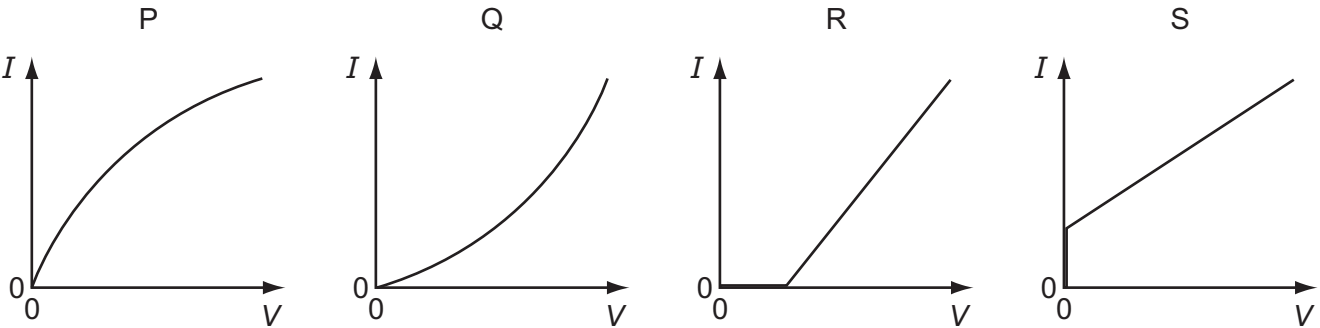


33 The graphs show possible current-voltage (I - V) relationships for a filament lamp and for a semiconductor diode.



Which row best specifies the correct I - V graphs for the lamp and the diode?

	filament lamp	semiconductor diode
A	P	R
B	P	S
C	Q	R
D	Q	S

Space for working