

34 A cell of e.m.f. E delivers a charge Q to an external circuit.

Which statement is correct?

- A** The energy dissipation in the external circuit is EQ .
- B** The energy dissipation within the cell is EQ .
- C** The external resistance is EQ .
- D** The total energy dissipation in the cell and the external circuit is EQ .