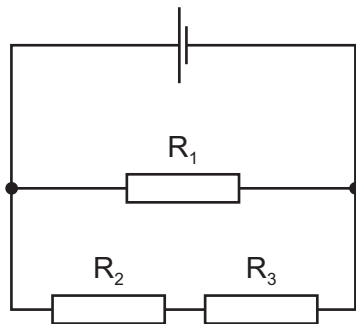


- 34 A cell of negligible internal resistance is connected to resistors R_1 , R_2 and R_3 , as shown. The cell provides power to the circuit and power is dissipated in the resistors.



Which word equation **must** be correct?

- A power loss in R_1 = power loss in R_2 + power loss in R_3
- B power loss in R_2 = power loss in R_3
- C power output of cell = power loss in R_1 + power loss in R_2 + power loss in R_3
- D power output of cell = power loss in R_1