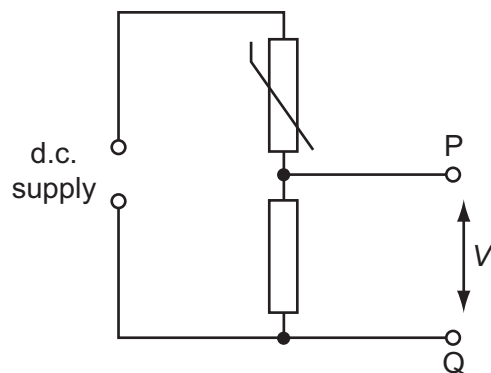
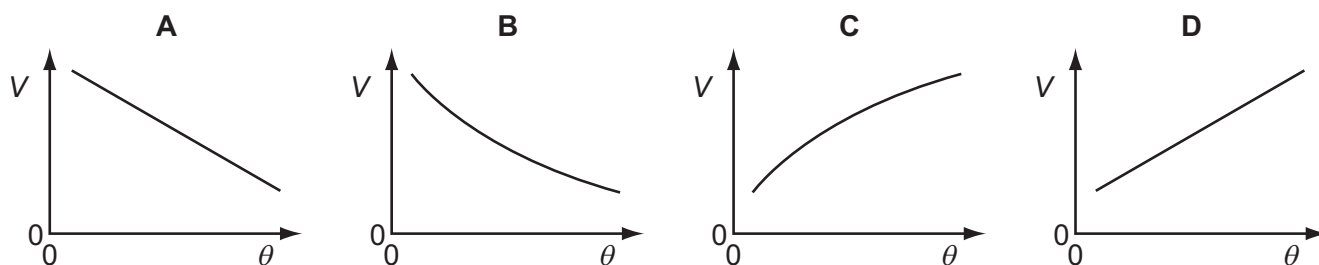


37 In the circuit shown, the resistance of the thermistor decreases as temperature increases.



Which graph shows the variation with Celsius temperature θ of potential difference V between points P and Q?



Space for working