

35 Three resistors are connected to a cell of negligible internal resistance.

Which circuit has a combined resistance of $100\ \Omega$?

