

36 The diagram shows four identical resistors connected in a circuit.

Which resistor dissipates the most power?

