

35 The potential difference across a component in a circuit is 2.0 V.

How many electrons must flow through this component in order for it to be supplied with 4.8 J of energy?

A 2.6×10^{18}

B 1.5×10^{19}

C 3.0×10^{19}

D 6.0×10^{19}

Space for working