

6 (a) Define electric potential difference.

.....
..... [1]

(b) A battery is connected to two resistors X and Y, as shown in Fig. 6.1.

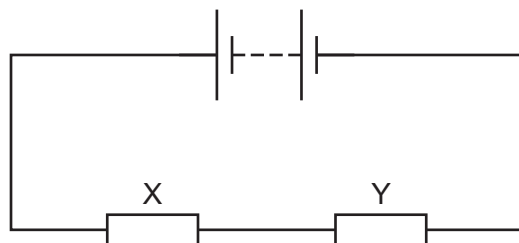


Fig. 6.1

The resistance of resistor X is greater than the resistance of resistor Y.

State and explain which resistor dissipates more power.

.....
.....
.....
..... [3]

(c) A battery of electromotive force (e.m.f.) 9.0V and internal resistance r is connected to two resistors P and Q, as shown in Fig. 6.2.

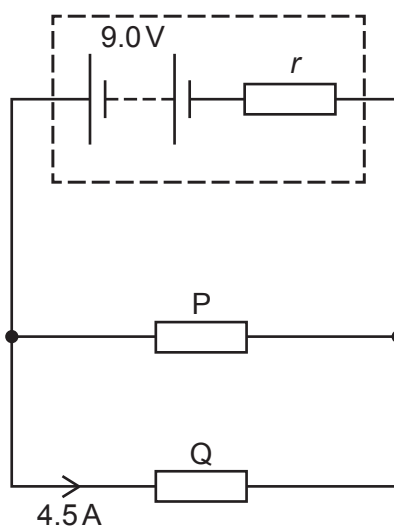


Fig. 6.2

A total charge of 650 C moves through resistor P in a time interval of 540 s. During this time resistor P dissipates 4800 J of energy. The current in resistor Q is 4.5 A. Assume that the e.m.f. of the battery remains constant.

Calculate:

- (i) the current in resistor P

current = A [2]

- (ii) the potential difference across resistor P

potential difference = V [2]

- (iii) the internal resistance r of the battery.

$r = \dots \Omega$ [2]