

- 36** Two resistors have a combined resistance of $34\ \Omega$ when connected in series. The same resistors have a combined resistance of $7.4\ \Omega$ when connected in parallel.

What is the resistance of one of the resistors?

A $15\ \Omega$

B $17\ \Omega$

C $23\ \Omega$

D $27\ \Omega$