

6 (a) (i) Define the *capacitance* of a parallel plate capacitor.

.....  
.....  
..... [2]

(ii) State **three** functions of capacitors in electrical circuits.

1. ....  
2. ....  
3. ..... [3]

(b) A student has available four capacitors, each of capacitance  $24\ \mu\text{F}$ .

The capacitors are connected as shown in Fig. 6.1.

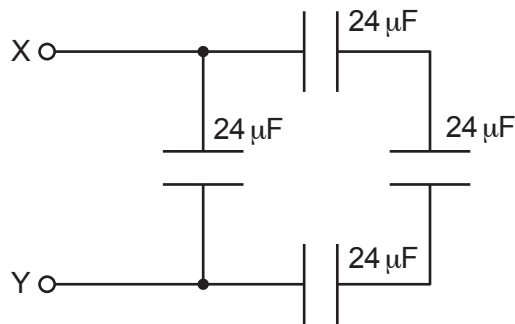


Fig. 6.1

Calculate the combined capacitance between the terminals X and Y.

capacitance = .....  $\mu\text{F}$  [2]