

- 8 A student has available some resistors, each of resistance  $100\ \Omega$ .
- (a) Draw circuit diagrams, one in each case, to show how a number of these resistors may be connected to produce a combined resistance of
- (i)  $200\ \Omega$ ,
- (ii)  $50\ \Omega$ ,
- (iii)  $40\ \Omega$ .

[4]

- (b) The arrangement of resistors shown in Fig. 8.1 is connected to a battery.

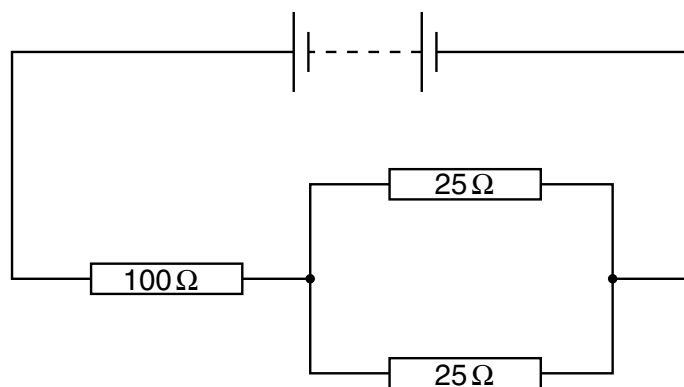


Fig. 8.1

The power dissipation in the  $100\ \Omega$  resistor is  $0.81\ \text{W}$ . Calculate

- (i) the current in the circuit,

current = ..... A

- (ii) the power dissipation in each of the  $25\ \Omega$  resistors.

power = ..... W

[4]