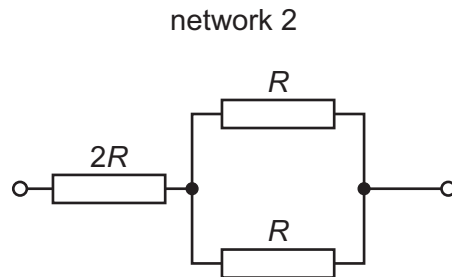
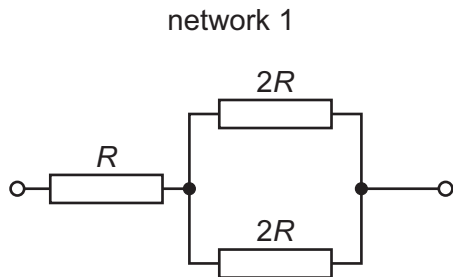


36 The diagram shows two resistor networks.



What is the ratio $\frac{\text{total resistance of network 1}}{\text{total resistance of network 2}}$?

A $\frac{4}{5}$

B $\frac{5}{4}$

C $\frac{1}{2}$

D $\frac{2}{1}$