

34 A filament lamp has a resistance of $180\ \Omega$ when the current in it is 500 mA .

What is the power transformed in the lamp?

A 45 W

B 50 W

C 90 W

D 1400 W

35 Two wires P and Q made of the same material are connected to the same electrical supply.