

31 There is a potential difference V across a resistor of resistance R . The current in the resistor is I .

Which equation gives the power P dissipated by the resistor?

A $P = V^2 I$

B $P = \frac{V^2}{I}$

C $P = V^2 R$

D $P = \frac{V^2}{R}$