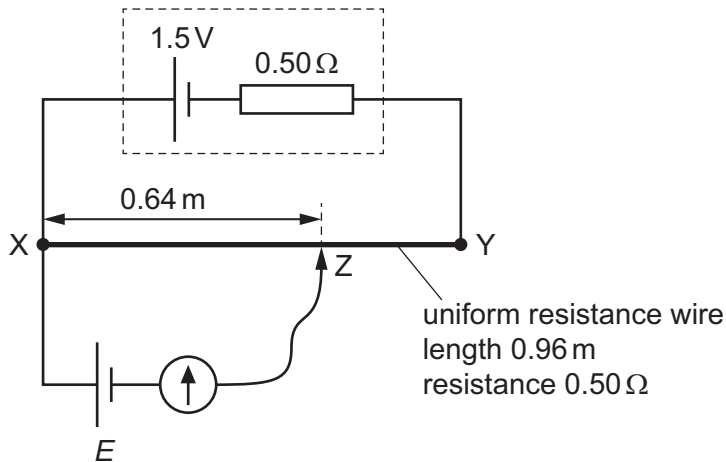


- 37** A potentiometer circuit is used to determine the electromotive force (e.m.f.) E of a cell. The circuit includes a second cell of e.m.f. 1.5 V and internal resistance $0.50\ \Omega$ that is connected to a uniform resistance wire XY , as shown.



The resistance wire XY has a length of 0.96 m and a resistance of $0.50\ \Omega$.

The movable connection Z is moved along wire XY . The galvanometer reading is zero when length XZ is 0.64 m .

What is the value of e.m.f. E ?

- A** 0.50 V **B** 0.75 V **C** 1.0 V **D** 1.1 V