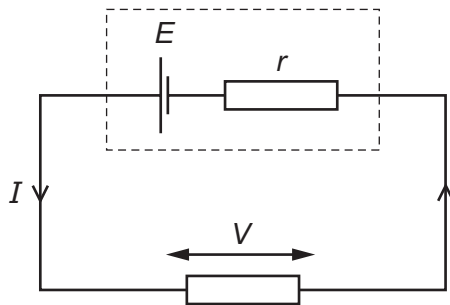


- 32** A cell of electromotive force  $E$  and internal resistance  $r$  is connected to an external resistor, as shown.



The current in the circuit is  $I$  and the potential difference (p.d.) across the external resistor is  $V$ .

In the equation  $(E - V) = Ir$ , what does the term  $(E - V)$  represent?

- A** electrical energy per unit charge lost in the cell
- B** electrical energy per unit charge lost in the complete circuit
- C** electrical energy per unit charge lost in the connecting wire
- D** electrical energy per unit charge lost in the external resistor