

- 6 (a) A wire has length 100cm and diameter 0.38mm. The metal of the wire has resistivity  $4.5 \times 10^{-7} \Omega \text{m}$ .

Show that the resistance of the wire is  $4.0 \Omega$ .

[3]

- (b) The ends B and D of the wire in (a) are connected to a cell X, as shown in Fig. 6.1.

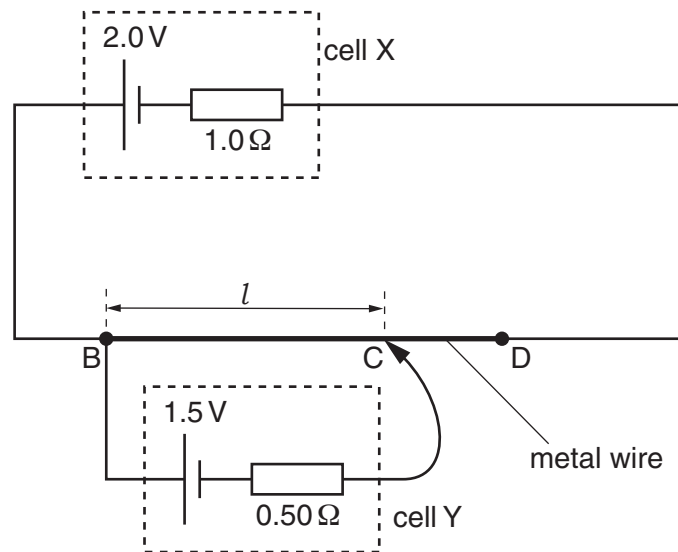


Fig. 6.1

The cell X has electromotive force (e.m.f.) 2.0V and internal resistance  $1.0 \Omega$ .

A cell Y of e.m.f. 1.5V and internal resistance  $0.50 \Omega$  is connected to the wire at points B and C, as shown in Fig. 6.1.

The point C is distance  $l$  from point B. The current in cell Y is zero.

Calculate

- (i) the current in cell X,

current = ..... A [2]

(ii) the potential difference (p.d.) across the wire BD,

p.d. = ..... V [1]

(iii) the distance  $l$ .

$l$  = ..... cm [2]

(c) The connection at C is moved so that  $l$  is increased. Explain why the e.m.f. of cell Y is less than its terminal p.d.

.....  
.....  
.....[2]