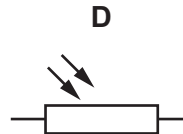
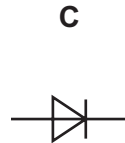
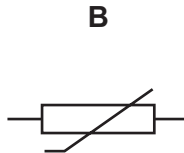
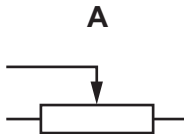


**32** Which symbol represents a component whose resistance is designed to change with temperature?



**33** In the circuit below, a voltmeter of resistance  $R_V$  and an ammeter of resistance  $R_A$  are used to