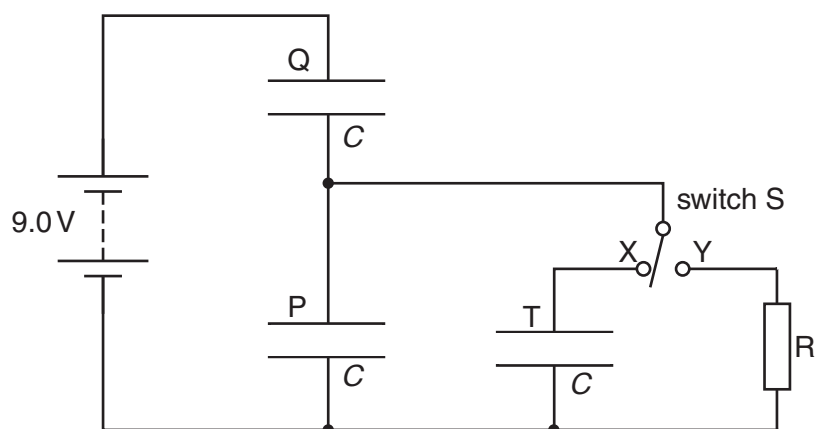


- 6 Two capacitors P and Q, each of capacitance  $C$ , are connected in series with a battery of e.m.f. 9.0 V, as shown in Fig. 6.1.



**Fig. 6.1**

A switch S is used to connect either a third capacitor T, also of capacitance  $C$ , or a resistor R, in parallel with capacitor P.

- (a)** Switch S is in position X.

Calculate

- (i)** the combined capacitance, in terms of  $C$ , of the three capacitors,

capacitance = ..... [2]

- (ii)** the potential difference across capacitor Q. Explain your working.

potential difference = ..... V [2]

- (b) Switch S is now moved to position Y.  
State what happens to the potential difference across capacitor P and across capacitor Q.

capacitor P: .....

.....

.....

capacitor Q: .....

.....

.....

[4]

[Total: 8]