

34 Which circuit symbol represents a microphone?

A



B



C



D



35

A circuit is shown below. The circuit contains a battery, a switch, a lamp and a buzzer. The switch is closed. The lamp is lit. The buzzer is not ringing.