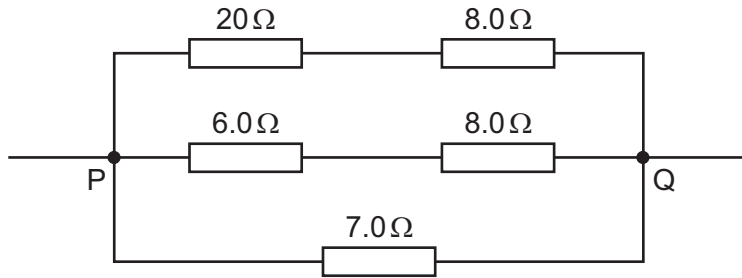


38 Five resistors are connected as shown.



What is the total resistance between points P and Q?

A $0.25\ \Omega$

B $0.61\ \Omega$

C $4.0\ \Omega$

D $16\ \Omega$