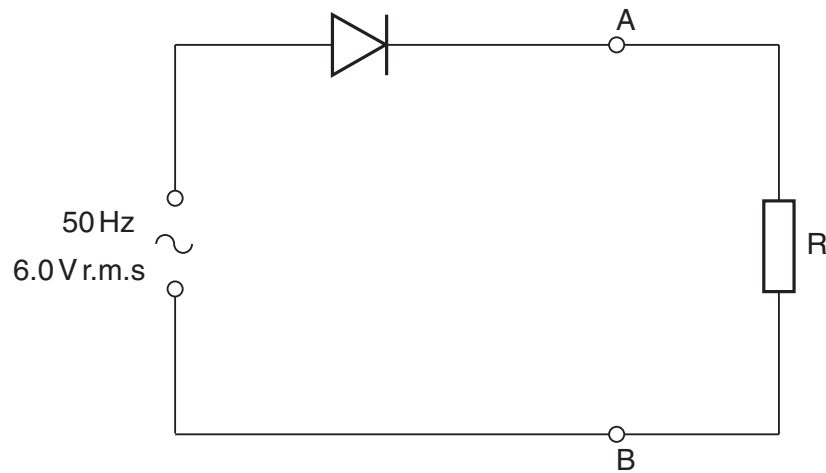


- 6 An alternating supply of frequency 50 Hz and having an output of 6.0 V r.m.s. is to be rectified so as to provide direct current for a resistor R. The circuit of Fig. 6.1 is used.



**Fig. 6.1**

The diode is ideal. The Y-plates of a cathode-ray oscilloscope (c.r.o.) are connected between points A and B.

- (a) (i) Calculate the maximum potential difference across the diode during one cycle.

potential difference = ..... V [2]


- (ii) State the potential difference across R when the diode has maximum potential difference across it. Give a reason for your answer.

.....  
 ..... [1]

- (b) The Y-plate sensitivity of the c.r.o. is set at  $2.0 \text{ V cm}^{-1}$  and the time-base at  $5.0 \text{ ms cm}^{-1}$ .

On Fig. 6.2, draw the waveform that is seen on the screen of the c.r.o.

[3]

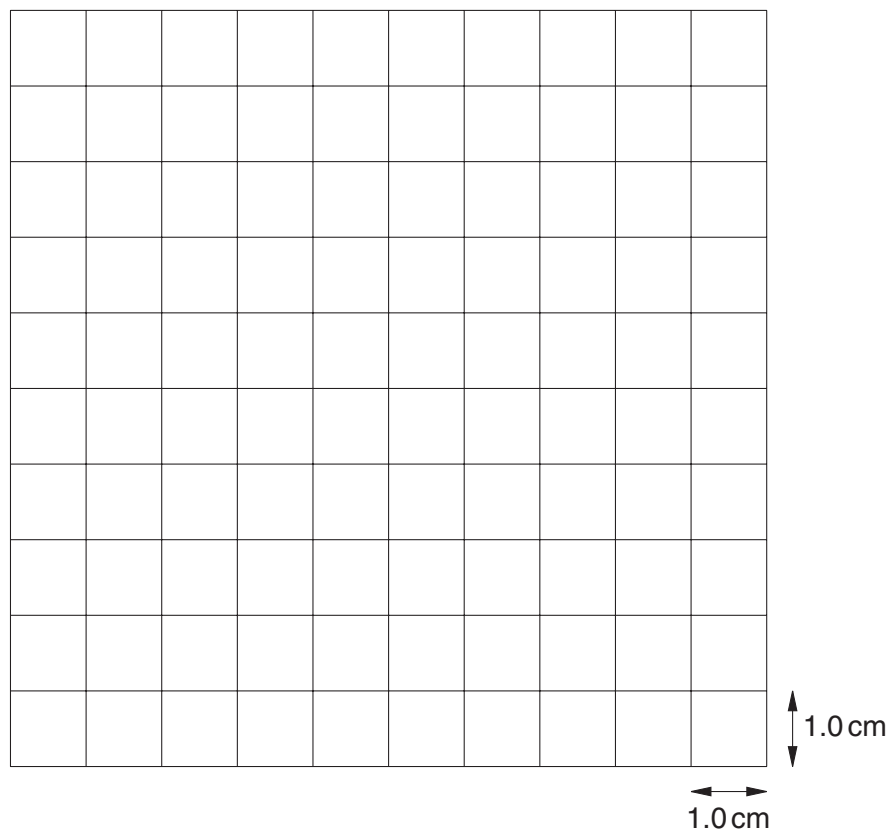

**Fig. 6.2**

- (c) A capacitor of capacitance  $180 \mu\text{F}$  is connected into the circuit to provide smoothing of the potential difference across the resistor R.

- (i) On Fig. 6.1, show the position of the capacitor in the circuit. [1]
- (ii) Calculate the energy stored in the fully-charged capacitor.

energy = ..... J [3]

- (iii) During discharge, the potential difference across the capacitor falls to  $0.43 V_0$ , where  $V_0$  is the maximum potential difference across the capacitor.

Calculate the fraction of the total energy that remains in the capacitor after the discharge.

fraction = ..... [2]