

36 A cell is connected to a resistor of resistance $3.00\ \Omega$. The current in the resistor is $1.00\ \text{A}$.

A second identical resistor is added in parallel. The current becomes $1.93\ \text{A}$.

What are the e.m.f. E and internal resistance r of the cell?

	E/V	r/Ω
A	0.113	3.11
B	3.04	0.0358
C	3.11	0.113
D	9.34	6.34

37 A battery with e.m.f. $12.0\ \text{V}$ and internal resistance $0.50\ \Omega$ is connected to a resistor of resistance $2.00\ \Omega$.