

- 5** Some capacitors are marked '48 μF , safe working voltage 25 V'.

Show how a number of these capacitors may be connected to provide a capacitor of capacitance

- (a)** 48 μF , safe working voltage 50 V,

[2]

- (b)** 72 μF , safe working voltage 25 V.

[2]