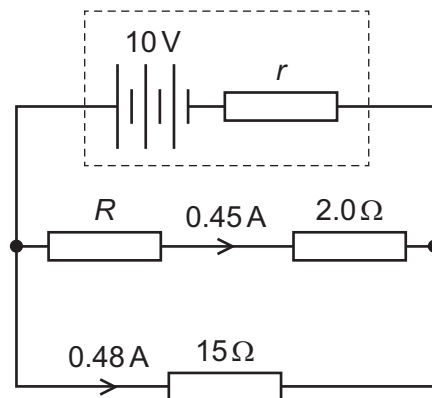


- 36** A battery of electromotive force (e.m.f.)  $10\text{ V}$  and internal resistance  $r$  is connected to three resistors of resistances  $R$ ,  $2.0\,\Omega$  and  $15\,\Omega$ , as shown. A current of  $0.45\text{ A}$  is in the resistor of resistance  $2.0\,\Omega$  and a current of  $0.48\text{ A}$  is in the resistor of resistance  $15\,\Omega$ .



What are the values of  $r$  and  $R$ ?

	$r/\Omega$	$R/\Omega$
<b>A</b>	3.0	14
<b>B</b>	3.0	20
<b>C</b>	5.8	14
<b>D</b>	5.8	20