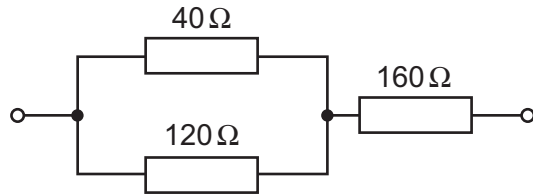


35 The diagram shows part of a circuit.



What is the total resistance of the combination of the three resistors?

A $320\ \Omega$

B $240\ \Omega$

C $190\ \Omega$

D $80\ \Omega$

36 The diagram shows an arrangement of resistors