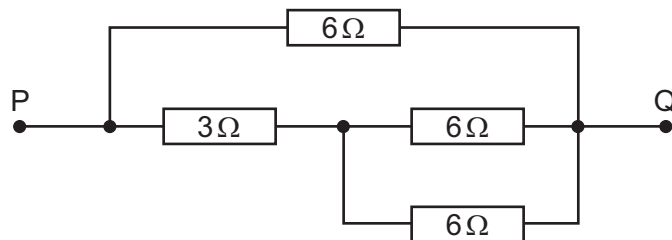


**38** The diagram shows a d.c. circuit.



What is the resistance between the points P and Q due to the resistance network?

**A**  $0.47\Omega$

**B**  $2.1\Omega$

**C**  $3.0\Omega$

**D**  $21\Omega$

**Space for working**